

Fall 2021

California State University, Northridge

Department of Electrical and Computer Engineering

Homework 0
September 8, 2021

ECE 524
Professor: Shahn timerzaei

Written By: Morris Blaustein

1. Design Source

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity barrel_shift is

Port (DIN : in STD_LOGIC_VECTOR (15 downto 0);
SHIFT_AMT : in STD_LOGIC_VECTOR (3 downto 0);
CLK : in STD_LOGIC;
ENB : in STD_LOGIC;
DOUT : out STD_LOGIC_VECTOR (15 downto 0));

end barrel_shift;

architecture Behavioral of barrel_shift is

signal patch1, patch2, patch4 : std_logic_vector(15 downto 0);

signal shift1, shift2, shift4, shift8 : std_logic;

begin

shift1 <= SHIFT_AMT(0);

shift2 <= SHIFT_AMT(1);

shift4 <= SHIFT_AMT(2);

shift8 <= SHIFT_AMT(3);

process (clk)

begin

if (clk'event and clk = '1') then

if ENB = '1' then

case shift1 is

when '0' => patch1 <= DIN;

when '1' => patch1 <= DIN(14 downto 0) & DIN(15);

when others => null;

end case;

case shift2 is

when '0' => patch2 <= patch1;

when '1' => patch2 <= patch1(13 downto 0) & patch1(15 downto 14);

when others => null;

end case;

case shift4 is

when '0' => patch4 <= patch2;

when '1' => patch4 <= patch2(11 downto 0) & patch2(15 downto 12);

when others => null;

end case;

case shift8 is

when '0' => DOUT <= patch4;

```

        when '1' => DOUT <= patch4(7 downto 0) & patch4(15 downto 8);
        when others => null;
    end case;
end if;
end if;

end process;
end Behavioral;

```

1. Simulation Source

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity tb_barrel_shift is
-- Port();
end tb_barrel_shift;

architecture Behavioral of tb_barrel_shift is
component barrel_shift is
    Port ( DIN : in STD_LOGIC_VECTOR (15 downto 0);
          SHIFT_AMT : in STD_LOGIC_VECTOR (3 downto 0);
          CLK : in STD_LOGIC;
          ENB : in STD_LOGIC;
          DOUT : out STD_LOGIC_VECTOR (15 downto 0));
end component barrel_shift;

signal DIN_tb, DOUT_tb : std_logic_vector(15 downto 0);
signal SHIFT_AMT_tb : std_logic_vector(3 downto 0);
signal CLK_tb, ENB_tb : std_logic;

constant CP: time := 10ns;

begin

uut : barrel_shift port map( DIN => DIN_tb, SHIFT_AMT => SHIFT_AMT_tb, CLK => CLK_tb, ENB =>
ENB_tb, DOUT => DOUT_tb );

process
begin
CLK_tb <= '1';
wait for CP/2;
CLK_tb <= '0';
wait for CP/2;
end process;


```

```

process
begin
DIN_tb <= "10000000000000000";
SHIFT_AMT_tb <= "1011";
wait for 20ns;
ENB_tb <= '1';
wait;
end process;
end Behavioral;

```

1. Simulation

 

2.

The following process will run whenever there is a change to CLK or RST. Thus, it will reset the flip flop to 0 regardless of the state of the clock when RST goes to 1.

```

process (CLK, RST)
begin
if (RST = '1') then
q <= '0';
end if;
if (CLK`event and CLK='1') then
q <= d;
end if;
end process;

```

3. Design Source

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity clk_div_2 is
    Port ( clk : in STD_LOGIC;
          div_clk : out STD_LOGIC);
end clk_div_2;

architecture Behavioral of clk_div_2 is

```

```
signal ct : integer:=0;
signal tmp : std_logic := '0';
```

```
begin
process(clk)
begin
if ( clk'event ) then
    ct <= ct + 1;
    if ( ct = 1 ) then
        tmp <= NOT tmp;
        ct <= 0;
    end if;
end if;
div_clk <= tmp;
```

```
end process;
end Behavioral;
```

3. Simulation Source

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity tb_clk_div_2 is
-- Port ( );
end tb_clk_div_2;
```

```
architecture Behavioral of tb_clk_div_2 is
component clk_div_2 is
    Port ( clk : in STD_LOGIC;
          div_clk : out STD_LOGIC);
end component clk_div_2;
```

```
signal clk_tb, div_clk_tb: STD_LOGIC;
```

```
constant CP : time:= 10ns;
```

```
begin
uut : clk_div_2 port map(clk => clk_tb, div_clk => div_clk_tb);
```

```
process
begin
clk_tb <= '1';
wait for CP/2;
```


```

clk_tb <= '0';
wait for CP/2;
end process;

end Behavioral;

```

3. Simulation

 

4. Design Source

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;

entity up_down_ctr is
    Port ( dir : in STD_LOGIC;
          reset : in STD_LOGIC;
          clk : in STD_LOGIC;
          clk_enb : in STD_LOGIC;
          load : in STD_LOGIC_VECTOR(7 downto 0);
          load_enb : in STD_LOGIC;
          output : out STD_LOGIC_VECTOR(7 downto 0));
end up_down_ctr;

architecture Behavioral of up_down_ctr is

begin
    process(clk,reset)
        variable count : integer := 0;
    begin
        if (reset = '1') then
            count := 0;
        elsif (rising_edge(clk) and clk_enb = '1') then
            if dir = '0' then
                count := count + 1;
                if count > 255 then
                    count := 0;
                end if;
            end if;
        end if;
    end process;
end Behavioral;

```

```

    end if;
    if dir = '1' then
        count := count - 1;
        if count < 0 then
            count := 255;
        end if;
    end if;
    if load_enb = '1' then
        count := to_integer(unsigned(load));
    end if;
end if;
output <= std_logic_vector(to_unsigned(count,output'length));
end process;
end Behavioral;

```

4. Simulation Source

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

entity tb_up_down_ctr is
-- Port ( );
end tb_up_down_ctr;

```

```

architecture Behavioral of tb_up_down_ctr is
component up_down_ctr is
    Port ( dir : in STD_LOGIC;
          reset : in STD_LOGIC;
          clk : in STD_LOGIC;
          clk_enb : in STD_LOGIC;
          load : in STD_LOGIC_VECTOR(7 downto 0);
          load_enb : in STD_LOGIC;
          output : out STD_LOGIC_VECTOR(7 downto 0));
end component up_down_ctr;

```

```

signal dir_tb, reset_tb, clk_tb, clk_enb_tb, load_enb_tb : std_logic;
signal load_tb, output_tb : std_logic_vector(7 downto 0);
constant CP : time := 10ns;

```

```

begin
    uut : up_down_ctr port map ( dir => dir_tb, reset => reset_tb, clk => clk_tb, clk_enb => clk_enb_tb, load
=> load_tb, load_enb => load_enb_tb, output => output_tb );

```

```

process
begin

```

```


clk_tb <= '1';
wait for CP/2;
clk_tb <= '0';
wait for CP/2;
end process;

process
begin
dir_tb <= '0';
reset_tb <= '0';
clk_enb_tb <= '1';
load_tb <= "11111110";
load_enb_tb <= '0';
wait for 10*CP;
load_enb_tb <= '1';
wait for CP;
load_enb_tb <= '0';
wait for 2*CP;
dir_tb <= '1';
wait for 10*CP;
wait;
end process;

end Behavioral;

```

4. Simulation

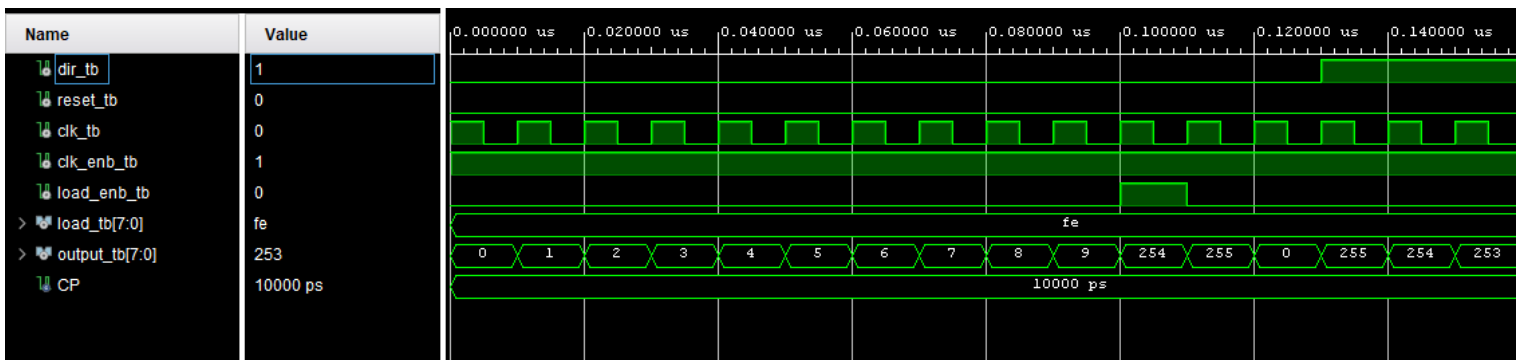

5. Design Source

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity fixed_clk is
    generic (num_cycles : integer := 1);

```



```

    Port ( clk : in STD_LOGIC;
           clk_out : out STD_LOGIC);
end fixed_clk;

```

architecture Behavioral of fixed_clk is

```

begin
process(clk)
variable temp : integer := 0;
variable temp2: std_logic := '0';
begin
if ( clk'event and clk='1' ) then
    temp := temp + 1;
end if;
if ( temp <= num_cycles ) then
    temp2 := not temp2;
end if;
clk_out <= temp2;
end process;

```

end Behavioral;

5. Simulation Source

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

entity tb_fixed_clk is
-- Port ( );
end tb_fixed_clk;

```

architecture Behavioral of tb_fixed_clk is

```

component fixed_clk is
    generic (num_cycles : integer);
    Port ( clk : in STD_LOGIC;
           clk_out : out STD_LOGIC);
end component fixed_clk;

```

```

signal clk_tb, clk_out_tb : STD_LOGIC;

```

```

constant n : time := 10ns;

```

```

begin
uut : fixed_clk generic map ( num_cycles =>30 )
    port map ( clk => clk_tb, clk_out => clk_out_tb );

```

```

process
begin
clk_tb <= '1';
wait for n/2;
clk_tb <= '0';
wait for n/2;
end process;


```

```

end Behavioral;

```

5. Simulation

 

6. Design Source

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

entity fib is
    Port ( clk : in STD_LOGIC;
          num_terms : in integer;
          output : out integer);
end fib;

```

```

architecture Behavioral of fib is

```

```

    signal x : integer;
    signal y : integer := 1;
    signal z : integer := 0;

```

```

begin
process (clk)
variable count : integer := 0;
begin
x <= y + z;
if (rising_edge(clk) and count < num_terms) then
    z <= y;
    y <= x;
    count := count + 1;

```

```
end if;  
end process;
```

```
output <= x;
```

```
end Behavioral;
```

6. Simulation Source

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity tb_fib is  
-- Port ( );  
end tb_fib;
```

```
architecture Behavioral of tb_fib is  
component fib is  
    Port ( clk : in STD_LOGIC;  
          num_terms : in integer;  
          output : out integer);  
end component fib;
```

```
signal clk_tb : std_logic;  
signal num_terms_tb, output_tb : integer;  
constant CP : time := 10ns;
```


```
begin  
uut : fib port map(clk=>clk_tb,num_terms=>num_terms_tb,output=>output_tb);
```

```
process  
begin  
clk_tb <= '0';  
wait for CP/2;  
clk_tb <= '1';  
wait for CP/2;  
end process;
```

```
process  
begin  
num_terms_tb <= 50;  
wait;  
end process;
```

```
end Behavioral;
```

6. Simulation

 

7. Design Source

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity seq_det is  
    Port ( input : in STD_LOGIC;  
          clk : in STD_LOGIC;  
          reset : in STD_LOGIC;  
          output : out STD_LOGIC);  
end seq_det;
```

architecture Behavioral of seq_det is

```
type state_type is (s0,s1,s2,s3);  
signal state, next_state : state_type;
```

```
begin  
process (clk,reset)  
begin  
if (reset ='1') then  
    state <= s0;  
elsif (rising_edge(clk)) then  
    state <= next_state;  
end if;  
end process;
```

```
process (state, input)  
begin  
case state is  
when s0 =>  
    output <= '0';  
    if (input = '0') then  
        next_state <= s0;  
    else
```


```

    next_state <= s1;
  end if;
when s1 =>
  output <= '0';
  if (input = '0') then
    next_state <= s2;
  end if;
when s2 =>
  output <= '0';
  if (input = '0') then
    next_state <= s0;
  else
    next_state <= s3;
  end if;
when s3 =>
  if (input = '0') then
    next_state <= s2;
    output <= '0';
  else
    next_state <= s1;
    output <= '1';
  end if;
end case;
end process;
end Behavioral;

```

 7.

Overlapping Mealy Machine "1011" Sequence Detector



7. Simulation Source

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity tb_seq_det is
-- Port ( );
end tb_seq_det;

architecture Behavioral of tb_seq_det is
component seq_det is
    Port ( input : in STD_LOGIC;
          clk : in STD_LOGIC;
          reset : in STD_LOGIC;
          output : out STD_LOGIC);
end component seq_det;

signal input_tb, clk_tb, reset_tb, output_tb : STD_LOGIC;\

constant t : time := 2ns;

begin
uut : seq_det port map ( input => input_tb, clk => clk_tb, reset => reset_tb, output => output_tb );

process
begin
clk_tb <= '1';
wait for t/2;
clk_tb <= '0';
wait for t/2;
end process;


process
begin
reset_tb <='1';
wait for t;
reset_tb <='0';
wait for t;
input_tb <= '1';
wait for t;
input_tb <= '0';
wait for t;
input_tb <= '1';
wait for t;
input_tb <= '1';
```

```

wait for t;
input_tb <= '0';
wait for t;
input_tb <= '1';
wait for t;
input_tb <= '1';
wait;
end process;
end Behavioral;

```

7. Simulation

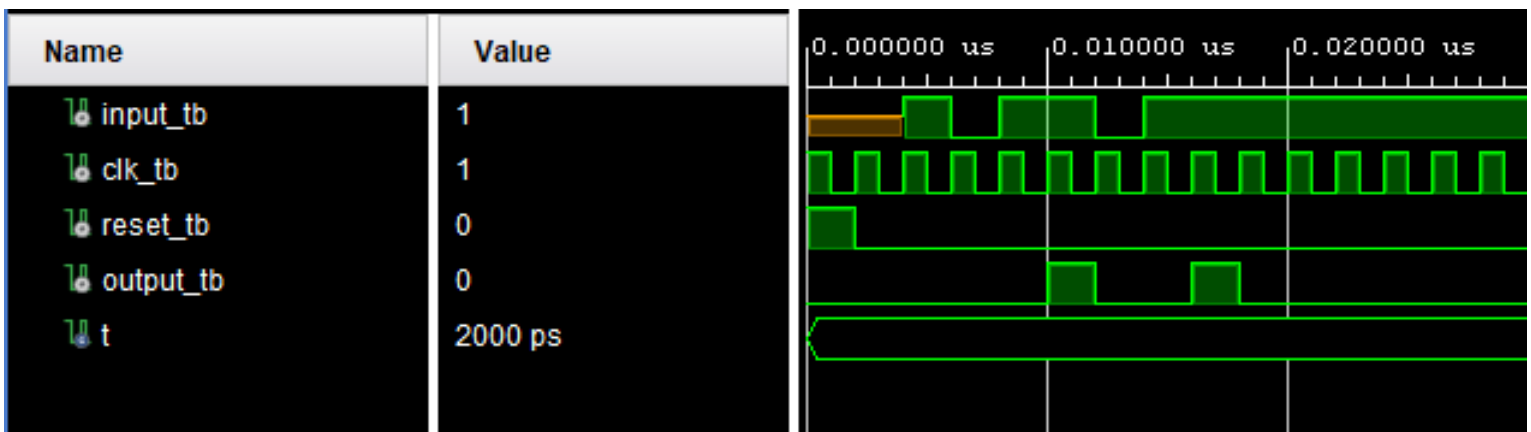

8. Design Source

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

entity exp is
    Port ( n : in integer;
          x : in integer;
          output : out integer);
end exp;

```

```

architecture Behavioral of exp is

```

```

    function NEXP( n : integer; x : integer )
        return integer is
    variable temp : integer := 1;
    begin
    for I in 1 to 100 loop
        if I <= x then
            temp := temp*n;

```

```

        end if;
    end loop;
    return temp;
end NEXP;

begin
    output <= NEXP(n,x);

end Behavioral;

```

8. Simulation Source

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity exp_tb is
    -- Port ( );
end exp_tb;

architecture Behavioral of exp_tb is
    component exp is
        Port ( n : in integer;
              x : in integer;
              output : out integer);
    end component exp;

    signal n_tb,x_tb,output_tb : integer;

begin
    uut : exp port map ( n => n_tb, x => x_tb, output => output_tb );

    process
    begin
        n_tb <= 5;
        x_tb <= 4;
        wait for 10ns;
        wait;
    end process;

end Behavioral;

```


8. Simulation

Name	Value	
n_tb	5	0.000000 us
x_tb	4	0.200000 us
output_tb	625	0.400000 us

9.

```
function COUNT_ZEROES( WORD : bit_vector(15 downto 0) )
    return integer is
    variable count : integer := 0;
begin
    for I in 0 to 15 loop
        if WORD(I) = '0' then
            count := count + 1;
        end if;
    end loop;
    return count;
end COUNT_ZEROES;
```

10.

```
function MAX( a : integer; b : integer )
    return integer is
begin
    if a > b then
        return a;
    else
        return b;
    end if;
end MAX;
```

11. Design Source

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity piso is
    Port ( mode : in STD_LOGIC_VECTOR (1 downto 0);
          input : in STD_LOGIC_VECTOR (7 downto 0);
          clk : in STD_LOGIC;
          rst : in STD_LOGIC;
```

```

        output : out STD_LOGIC);
end piso;

architecture Behavioral of piso is

    signal reg : STD_LOGIC_VECTOR(7 downto 0);

begin
    process(clk,rst)
        variable index : integer := 0;
    begin
        if rising_edge(clk) then
            if ( rst = '1' ) then
                reg <= ( others => '0' );
                output <= '0';
                index := 0;
            else
                case mode is
                    when "00" =>
                        reg <= input;
                        index := 0;
                    when "01" =>
                        if index < 8 then
                            output <= reg(index);
                            index := index + 1;
                        end if;
                        when others => null;
                    end case;
                end if;
                if index = 8 then
                    output <= '0';
                end if;
            end if;
        end process;
    end Behavioral;

```

11. Simulation Source

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity piso_tb is
-- Port ( );
end piso_tb;

```

architecture Behavioral of piso_tb is

component piso is

```
Port ( mode : in STD_LOGIC_VECTOR (1 downto 0);  
      input : in STD_LOGIC_VECTOR (7 downto 0);  
      clk : in STD_LOGIC;  
      rst : in STD_LOGIC;  
      output : out STD_LOGIC);
```

end component piso;

```
signal mode_tb : std_logic_vector(1 downto 0);
```

```
signal input_tb : std_logic_vector(7 downto 0);
```

```
signal clk_tb, rst_tb, output_tb : std_logic;
```

```
constant CP : time := 10ns;
```

```
begin
```

```
uut : piso port map( mode => mode_tb, input => input_tb, clk => clk_tb, rst => rst_tb, output =>  
output_tb);
```

```
process
```

```
begin
```

```
clk_tb <= '0';
```

```
wait for CP/2;
```

```
clk_tb <= '1';
```

```
wait for CP/2;
```

```
end process;
```

```
process
```

```
begin
```

```
rst_tb <= '0';
```

```
input_tb <= "10101010";
```

```
mode_tb <= "00";
```

```
wait for CP;
```

```
mode_tb <= "01";
```

```
wait for 8*CP;
```

```
input_tb <= "11110000";
```

```
mode_tb <= "00";
```

```
wait for CP;
```

```
mode_tb <= "01";
```


```
wait for 8*CP;
```

```
wait;
```

```
end process;
```

```
end Behavioral;
```

11. Simulation

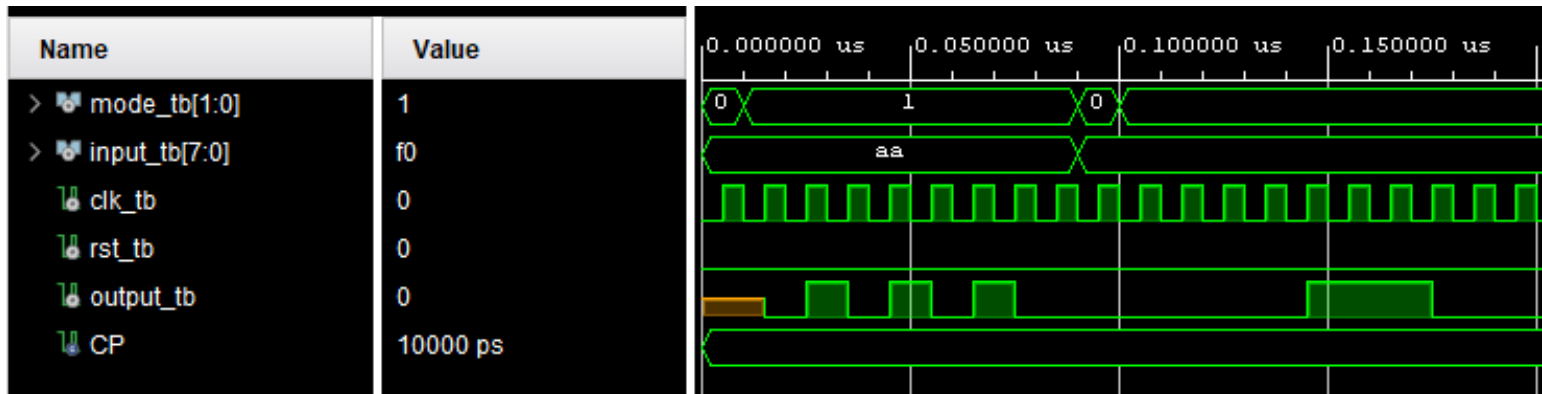

12.

```
constant PERIOD : time := 10ns;  
constant DUTY_CYCLE : time := 2ns;  
process  
begin  
  clk_tb <= '0';  
  wait for (PERIOD - DUTY_CYCLE);  
  clk_tb <= '1';  
  wait for DUTY_CYCLE;  
end process;
```

13.

```
function PARITY( a: std_logic_vector(31 downto 0) )  
  return std_logic us  
variable parity : std_logic := '0';  
begin  
  for I in a'range loop  
    parity := parity xor a(i);  
  end loop  
  return parity; --returns 1 if a has even parity  
end PARITY;
```